

Drive for better vision



Wildlife.ai WW500 Circuit Modification


Feb 25, 2025

Himax Technologies, Inc.
奇景光電股份有限公司

Load Switch C_T

1. DPD mode issue (1V8_WE/3V3_WE)

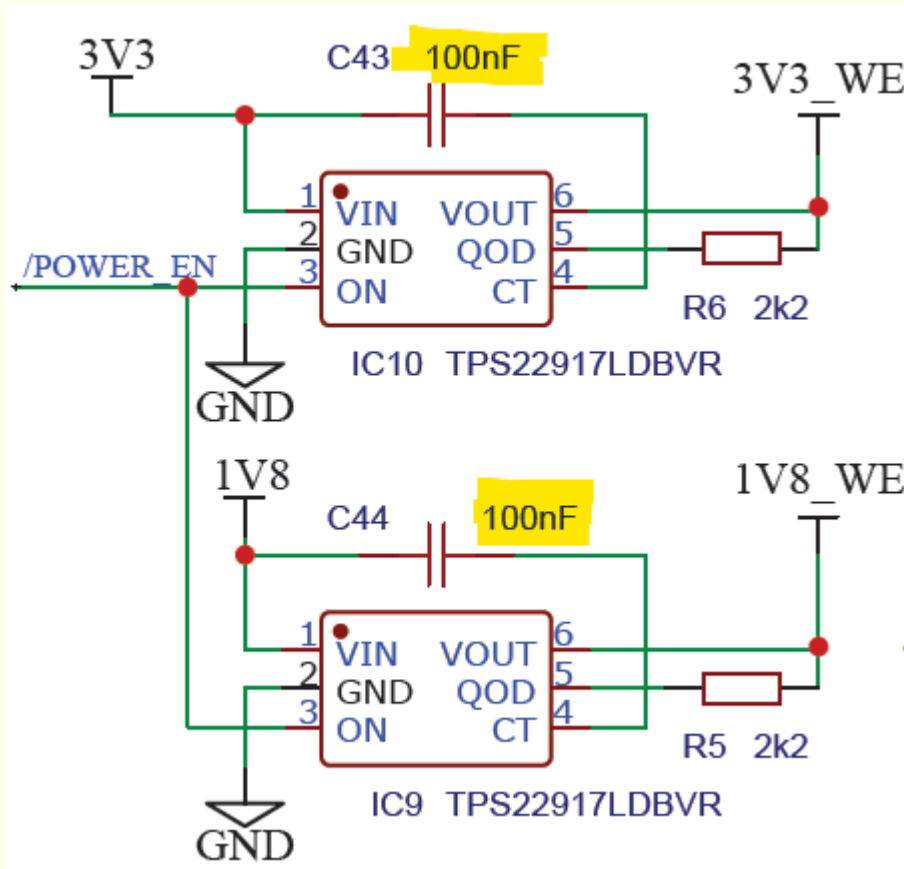a. 1V8_WE/3V3_WE switch capacitor : C43, C44 -> 1nF



- Adjustable turn ON limits inrush current (t_{ON}):
 - 5-V $t_{ON} = 100 \mu s$ at $72 \text{ mV}/\mu s$ ($C_T = \text{open}$)
 - 5-V $t_{ON} = 4000 \mu s$ at $2.3 \text{ mV}/\mu s$ ($C_T = 1000 \text{ pF}$)

CIS I2C Pull High



2. HM0360 I2C issue

- a. HM0360 SEN_SCL/SEN_SDA need to add pull-up resistors




HM0360 Always On Setting

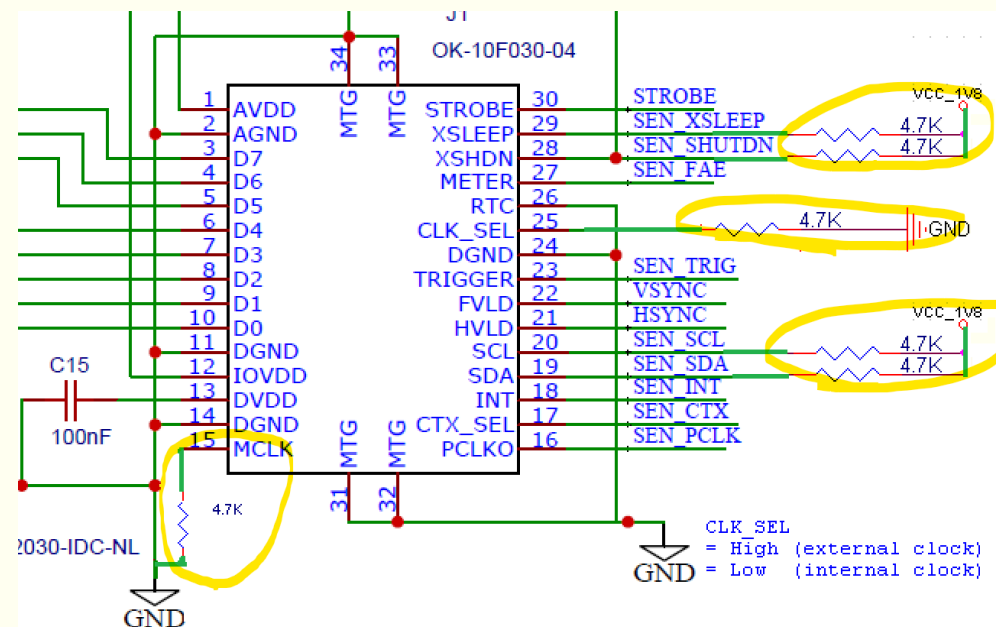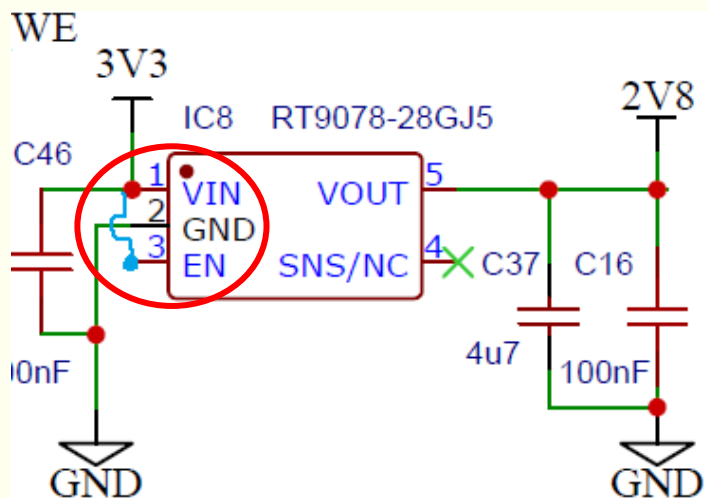3. HM0360 should be always on
 - a. HM0360 2V8 always on
 - b. HM0360 XSLEEP/XSHDN should be pull-high (always on)
 - c. WE2 SEN_XSLEEP/SEN_GPIO should be NC
4. HM0360 should be set the oscillator mode
 - a. HM0360 CLK_SEL/MCLK connect to DGND (OSC mode)
 - b. WE2 SEN_MCLK should be NC



HM0360 Always On Setting @WE2

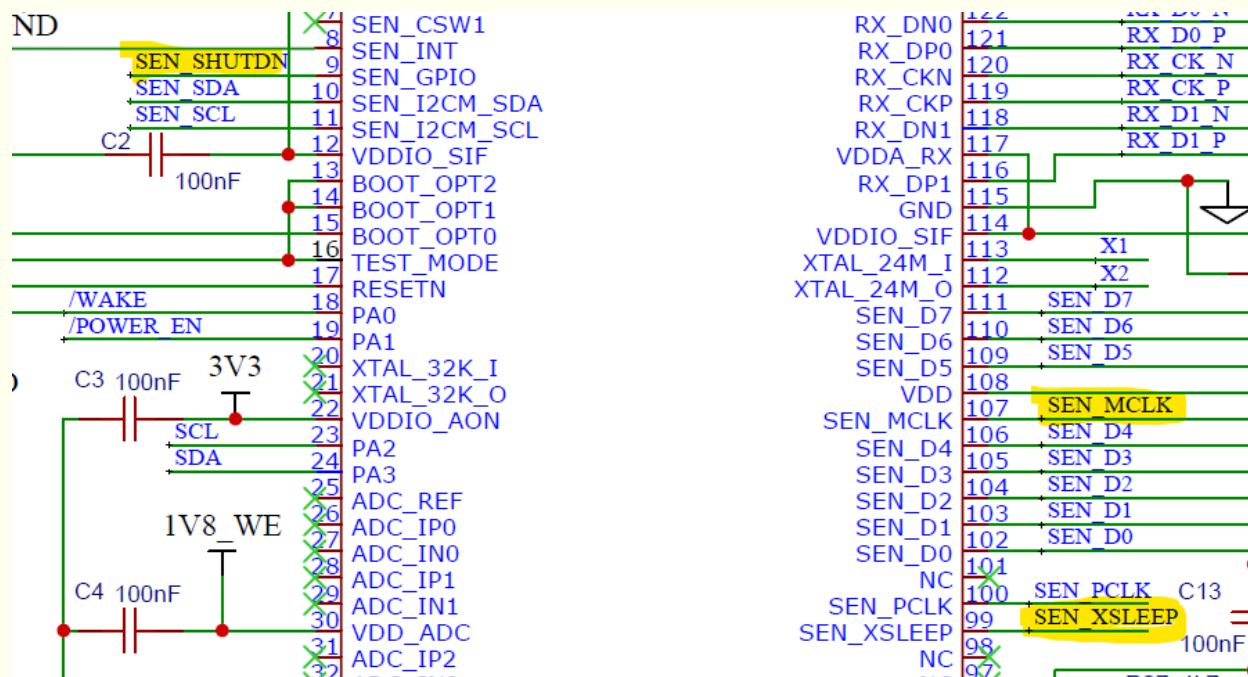
3. HM0360 should be always on
 - a. HM0360 2V8 always on
 - b. HM0360 XSLEEP/XSHDN should be pull-high (always on)
 - c. WE2 SEN_XSLEEP/SEN_GPIO should be NC
4. HM0360 should be set the oscillator mode
 - a. HM0360 CLK_SEL/MCLK connect to DGND (OSC mode)
 - b. WE2 SEN_MCLK should be NC



SEN_INT Signal State

5. HM0360 interrupt to WE2 issue

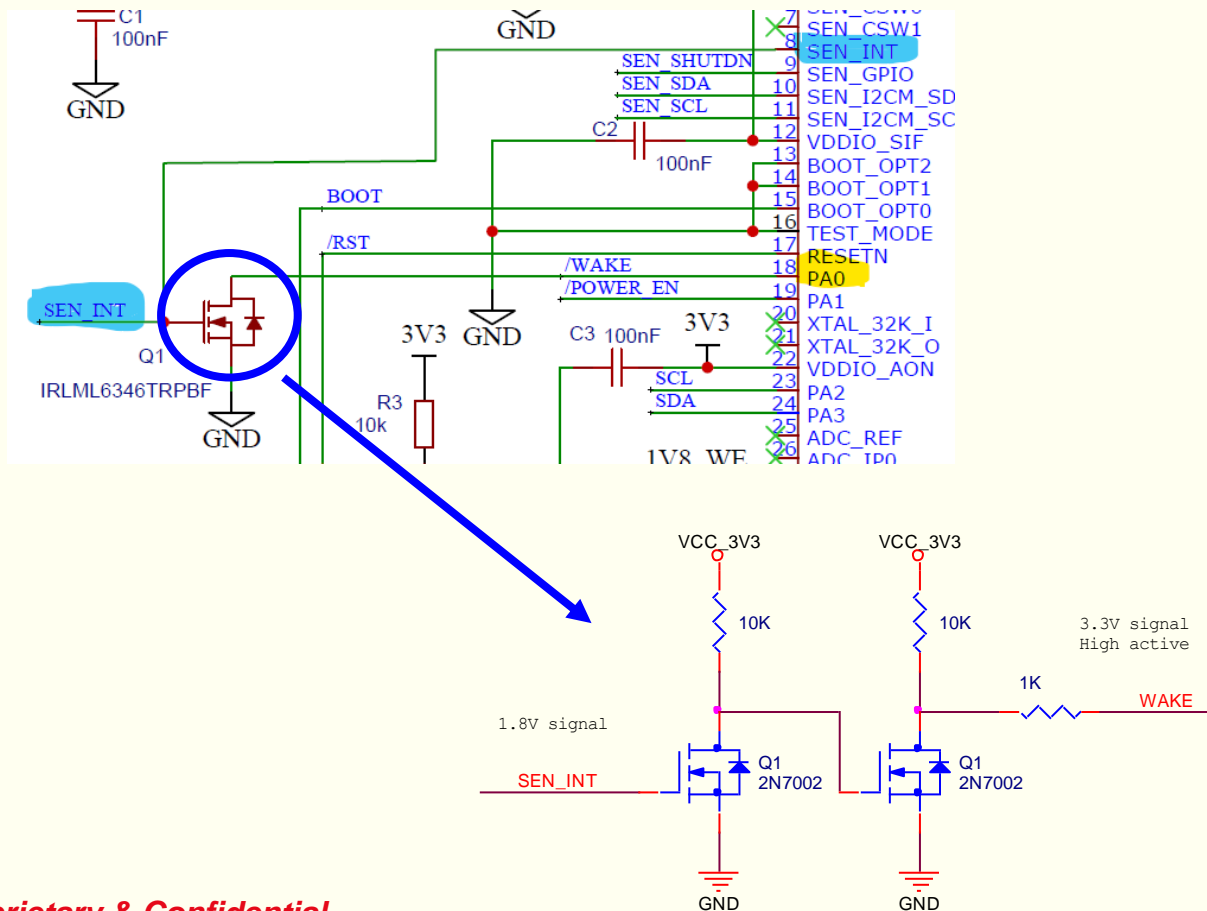a. Add level shift circuit (1.8V to 3.3V) between HM0360 INT(1.8V) and WE2 PA0(3.3V)





Drive for better vision